

INSTRUCTIONS: (i) Create a folder on desktop, rename it to your IDNO. (ii) Rename the project with your IDNO (iii) Write your IDNO and name in .v file. Write all modules in a single .v file. Put this .v file in the folder you created on desktop.

On command prompt type and run the following command to set the path:

set path=%PATH%;C:\iverilog\bin;C:\iverilog\gtkwave\bin

Q. A digital circuit is to be designed with the following specifications: At power on the circuit is in some initial state  $T_0$  and remains in that state till a START signal is received. Upon receiving the start signal a 4-bit counter, A, and a Flipflop G are initialized to zero and the circuit goes to next state  $T_1$ . In this state an external input X is checked on every clock edge and if found to be '1' then the counter is incremented by 1 at the same clock edge and the circuit goes to  $T_2$ . If X is zero, then the counter is not incremented and circuit remains in  $T_1$ . In  $T_2$  the counter output is checked for maximum value (1111) (Assume that a signal 'Z' if equal to 1 indicates that the counter has reached maximum value). If the output of counter is found to be '1111' then G is set to 1 in the same clock cycle and the operation stops. If the counter value is not '1111' then depending on value of X the operation continues.

The Block diagram and the ASM chart of the circuit is shown below in Fig1. and Fig 2.

 


Fig 1.

 


Fig 2.

The control logic circuit is shown in Fig3 below.


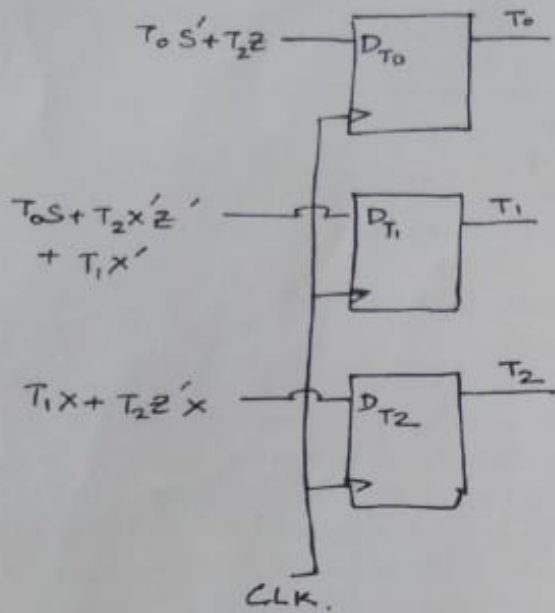


Fig 3

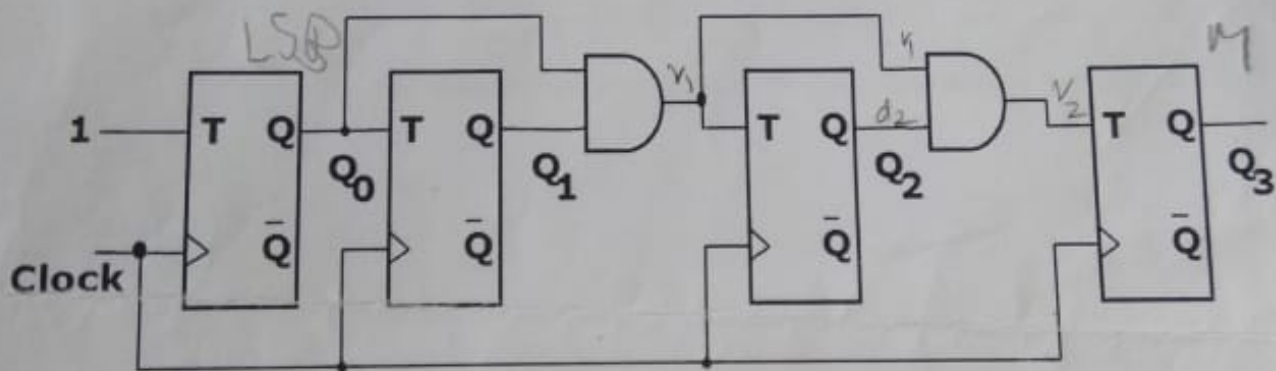

4-bit synchronous up counter

Fig.4

Implement the circuit in different modules stated as follows:

- (1) **ControlLogic:** This module takes as input  $S, Z, X$  and  $CLK$  and outputs three states  $T_0, T_1$  and  $T_2$ . The circuit diagram for the control logic is given above in Fig3. Implement the circuit using **gate level modeling**. Also write sub modules for d-ff (). d\_ff() can be implemented in behavioral modeling.
- (2) **TFF:** This module implements the functionality of a T-Flip flop with a synchronous clear. Implement this module using behavioral modeling.
- (3) **COUNTER\_4BIT:** This module implements the functionality of a 4-bit synchronous binary UP counter with a synchronous clear. Implement this module as shown in Fig4. above. Use TFF modules for your implementation.
- (4) **INTG:** This module integrates the above modules as per the datapath shown above in Fig 1. The inputs to this module are  $S$  and  $CLK$  and outputs are counter values and  $G$ .
- (5) **Testbench:** With  $S=1$  and  $X=1$  apply a clock of 1KHz and check the output of counter and  $G$ .